



Centre for Electronic Design and Technology
Netaji Subhas University of Technology , New Delhi

Electronic Electroscope

By Talha Parvez and Dhruv Saini

Date: DECEMBER 2023

Contents

1	Synopsis	1
2	Introduction	2
3	Circuit Schematic	3
4	Building Blocks of the Electroscope	4
4.1	<u>LOW BATTERY DETECTOR</u>	4
4.2	<u>BOOST CIRCUIT</u>	4
4.3	<u>VOLTAGE INVERTER</u>	5
4.4	<u>CHARGE AMPLIFIER</u>	5
4.5	<u>ARDUINO NANO</u>	6
5	Working	7
6	Bill Of Material[BOM]	9
7	End Result	10
8	Bibliography	12

1. Synopsis

In the realm of scientific instrumentation, the electroscope has long been an invaluable tool for detecting and measuring electric charges. Traditionally, the electroscope was constructed using metal foils or leaves suspended within an insulated container. When an electric charge was introduced to the electroscope, the leaves would repel each other, providing a visual indication of the presence of the charge.

With enhancements in technology, the classic electroscope has not been an optimal option for the transfer of information. So, we devised an " Electronic Electroscope " which is the second version of this series.

In this variant, the basic design idea for the project is :

- Analog block, that is used for the detection of charge and converting it into the voltage of the same polarity.
- Arduino Nano, which is used to convert analog data into digital data and map the digital data with random values which will then be used to multiplex a certain number of LEDs.
- Bar Graph LEDs, its used to display the multiplexed LEDs according to the magnitude of charge.

2. Introduction

In the field of Electronics, charge is a general term used very commonly. So, it's crucial to detect whether a body is charged or not, and if it's charged then identifying the polarity is significant information. Here comes the concept of **ELECTROSCOPE**, which is used to detect charge and its polarity. The block diagram for the implementation of the Electroscope is :

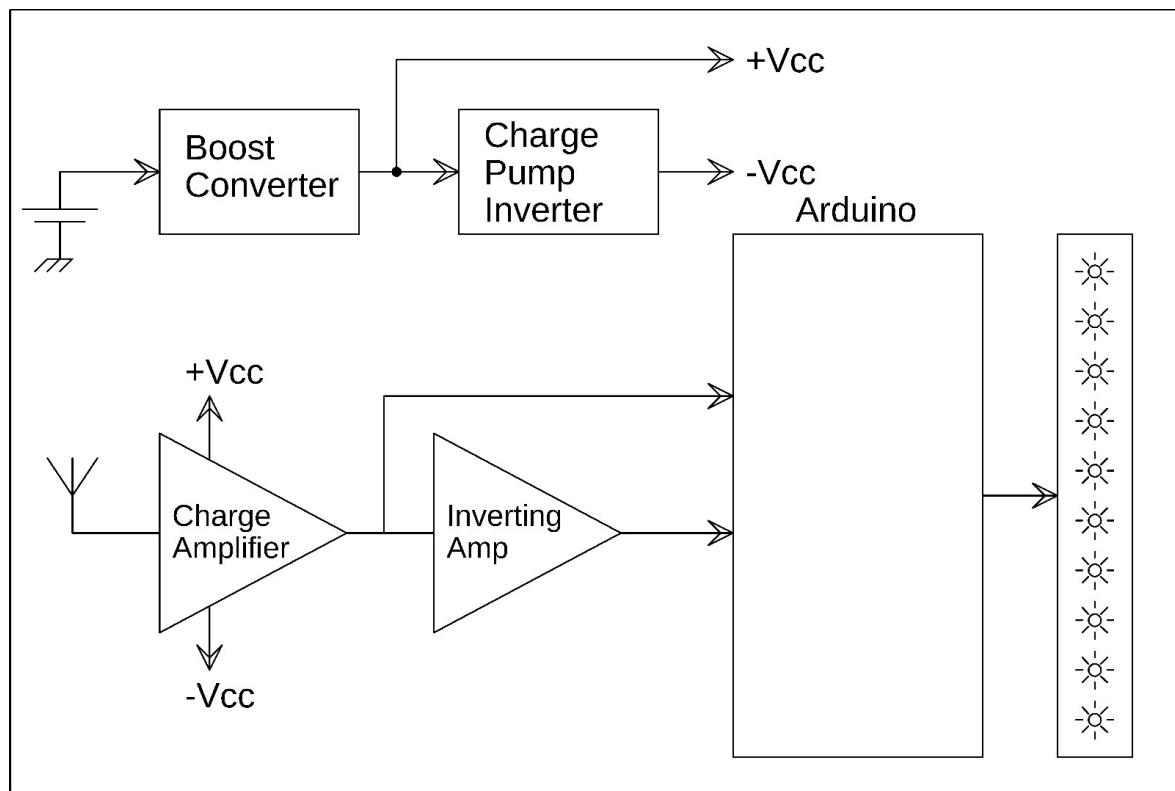


Figure 1: Block Diagram Of Electroscope

3. Circuit Schematic

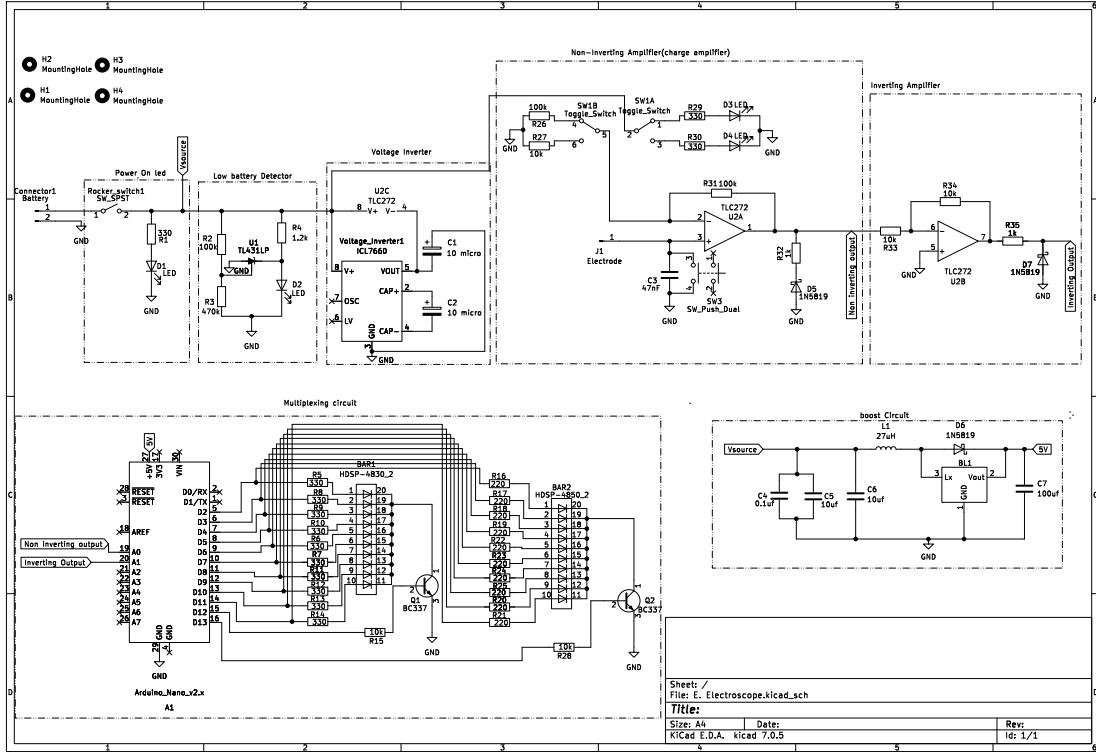


Figure 2: Circuit Schematic

4. Building Blocks of the ElectroScope

Firstly, we need to be familiar with the major working blocks of the project,

• 4.1 LOW BATTERY DETECTOR

- This circuit alerts the user when the battery needs charging. We have chosen the simplest way of determining that the battery capacity is low, and that's using the battery terminal voltage. This circuit lights up a warning LED whenever the voltage drops below a certain value.
- A circuit was constructed using TLC 431 (Precision Programmable Reference) and a couple of resistors that were used to glow the LED indicating a low battery level.

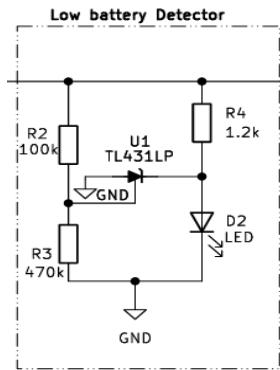


Figure 3: Low Battery Detector

• 4.2 BOOST CIRCUIT

- This circuit is a type of DC-DC (direct current to direct current) converter that takes an input voltage and produces a higher output voltage. It's designed to "Boost" or increase the voltage level from the input to the output.
- The Boost circuit used in this project is;

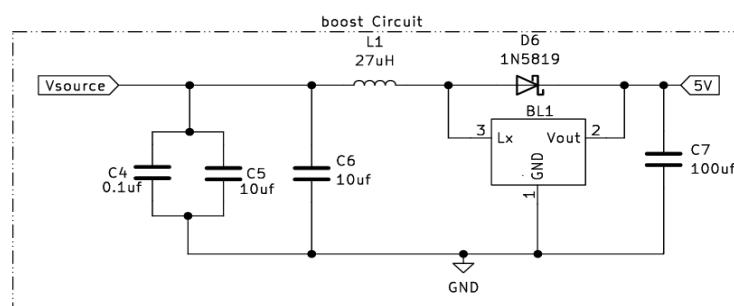


Figure 4: The Boost Circuit

4.3 VOLTAGE INVERTER

- A voltage inverter is a simple circuit that converts the positive voltage into negative voltage and vice versa, this circuit was implemented using TJ7660 IC, 2 X 10 uf capacitors, and a couple of jumpers.

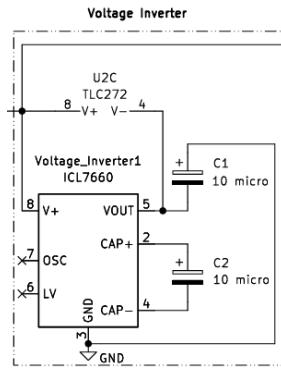


Figure 5: Voltage Inverter

• 4.4 CHARGE AMPLIFIER

- A charge amplifier is an electronic current integrator that produces a voltage output proportional to the integrated value of the input current, or the total charge injected.

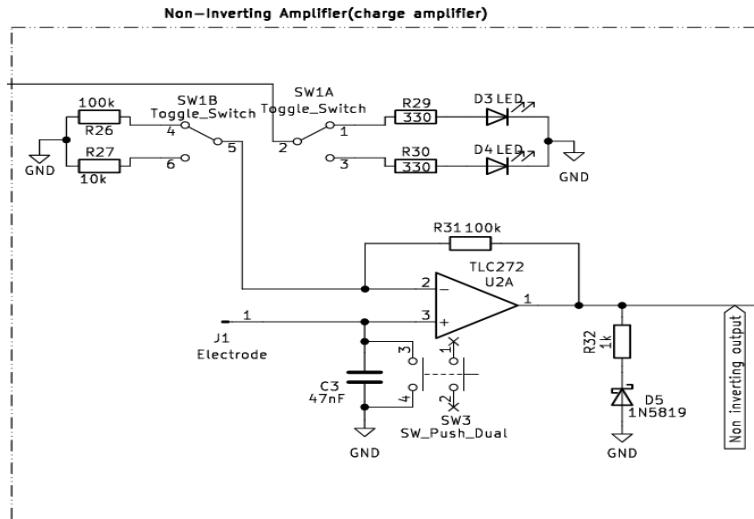


Figure 6: Charge Amplifier Circuit

• 4.5 ARDUINO NANO

- The Arduino Nano is a compact and versatile development board that is based on the ATmega328P microcontroller, which is the same chip used in the Arduino Uno board.
- The Nano is commonly used in various projects due to its small size, ease of use, and versatility. It's ideal for applications where space is limited, and it's used by hobbyists, makers, and professionals for a wide range of electronic projects.
- In this project, the Arduino Nano is used for multiplexing bar graph LEDs according to the input voltage fed to Arduino Nano.
- The connection of Arduino Nano With Bar Graph LEDs for multiplexing is;

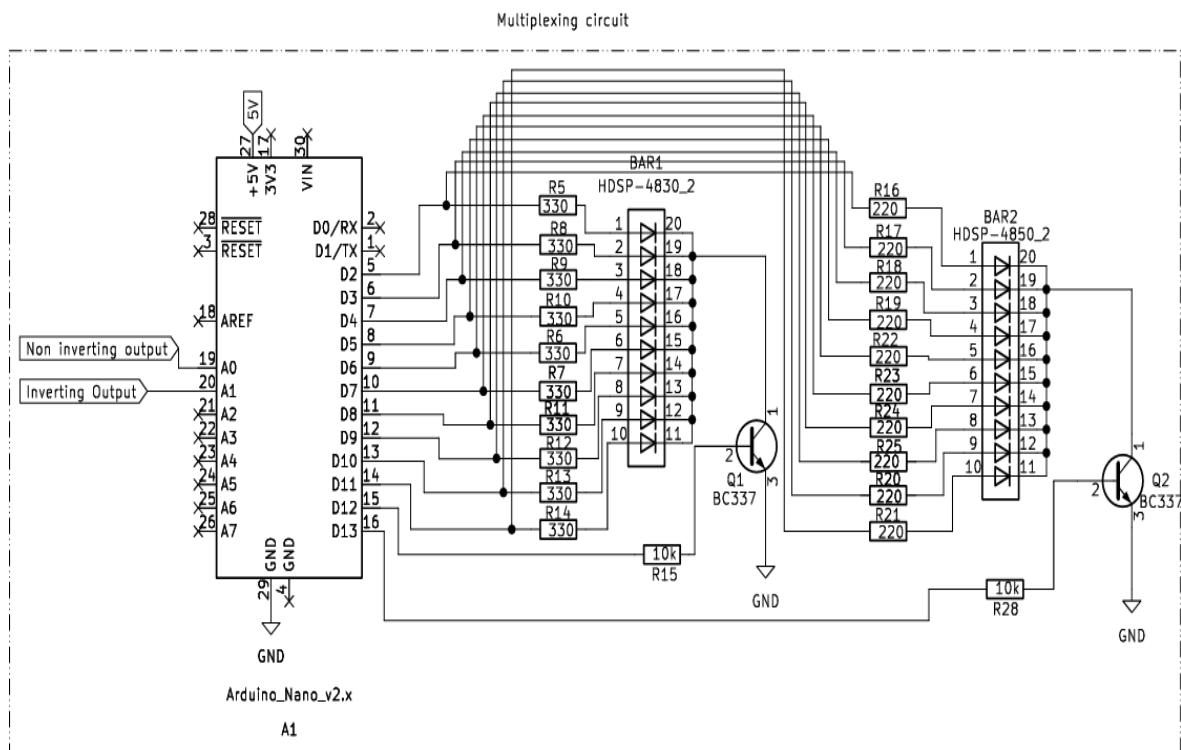


Figure 7: Multiplexing Circuit

5. Working

In this Project, we have used a lithium polymer battery to power the circuit. First Current goes into a Power on LED circuit, afterwards the current goes into a Low Battery Detector circuit to detect when the voltage goes below a specific level(Particularly 3.1 V) to remind the User to recharge the battery. The next step is to boost the voltage using a Boost Voltage regulator circuit designed using IC BL8530, its used to provide supply voltage to Arduino. Furthermore, the voltage is inverted using a Voltage Inverter circuit to provide the biasing voltage across the operational Amplifier (as the operational amplifiers require both positive and negative voltage for biasing to operate). Now, when the static charge is transferred to the non-inverting pin of the op-amp, the capacitor connected to the same leg gets charged, which provides voltage at the input. after which a voltage is developed at the output of the operational amplifier (a Non-Inverting amplifier), which is further fed to the Arduino NANO which turns on a specific number of bar graph LEDs of green color when a positive charge is given and LEDs of red color when a negative charge is given. The number of LEDs at the same charge can be altered using the gain Charge Amplifier, which is controlled using a Double Pole Double Throw (DPDT) Toggle switch.

```
1 void setup() {
2     pinMode(buzzerPin, OUTPUT);
3 }
4
5 // here we just incrementally change the number of the LED to be turned
6 // on.
7 void loop()
8 {
9
10    int analog_read1;
11    int analog_read2;
12    int value1, value2;
13    bool raw;                                // raw variable is used to
14    // identify which type of charge is being read at input
15    analog_read1 = analogRead(A0);
16    analog_read2 = analogRead(A1);
17    value1 = (analog_read1 * 4) / 1024;
18    value2 = (analog_read2 * 4) / 1024;
19    // Mapping for LEDs for specific amount of charge on different Pins
20    // of NANO
21    int onnA = map(analog_read1, 0, 1023, 0, 10);
22    int onnB = map(analog_read2, 0, 1023, 0, 10);
23
24    if (value1 > 0) {
25        raw = true;
26    }
27    else if (value2 > 0) {
28        raw = false;
29    }
30
31    noTone(buzzerPin);
```

```

30 if (raw == true)      // Turning ON LEDs (according to mapping) when
31   charge is being read by PIN A0 of NANO
32 {
33   if (onnA > 0 && onnA < 0.5) {
34     tone(buzzerPin, 350);
35   }
36   else {
37     for (int l = 0; l < onnA; l++)
38     {
39       lightOffB();
40       lightOnA(l);
41       delay(15 / onnA);
42       tone(buzzerPin, 350);
43     };
44     lightOffA();    // Turning OFF all the LEDs
45
46     noTone(buzzerPin);
47   }
48 }
49 noTone(buzzerPin);
50 if (raw == false)      // Turning ON LEDs when charge is being read
51   by PIN A1 of NANO
52 {
53   if (onnB > 0 && onnB < 0.5) {
54     tone(buzzerPin, 680);
55   }
56   else {
57     for (int f = 0; f < onnB; f++)
58     {
59       lightOffA();
60       lightOnB(f);
61       delay(15 / onnB);
62       tone(buzzerPin, 680);
63     };
64     lightOffB();    // Turning OFF all the LEDs
65     noTone(buzzerPin);
66   }
67 }
68 noTone(buzzerPin);
69 };

```

Code extraction 1: Multiplexing

6. Bill Of Material[BOM]

The list of components required for producing the Electroscope is given in the figure below,

Component List			
Resistors R1 = 330 R2 = 100k R3 = 470k R4 = 1.2k R5 - R14= 330 R15 = 4.7k R16 - R25 = 220 R26 = 100k R27 = 10k R28 = 10k R29 - R30 = 330 R31 = 100k R32 = 1k R33 - R34 = 10k R35 = 1k	Capacitors C1=10uf C2=10uf C3=47nf C4=0.1uf C5=10uf C6=10uf C7=100uf	Integrated Circuits IC1=TLC 272 BC IC2=TJ7660 IC3=TL431 IC4 =BL8530 Inductor L1 = 27uH Bar Graph LEDs BAR1 = Red BAR2 = Green	Miscellaneous 1x DPDT 2x Pin Molex connector X2 3x Schottky Diode [1N5859] Slider Switch Lithium polymer battery Copper wire Electrode 2x NPN Transistor [BC337] ATMega 328 based Arduino NANO

Figure 8: Bill Of Material

7. End Result

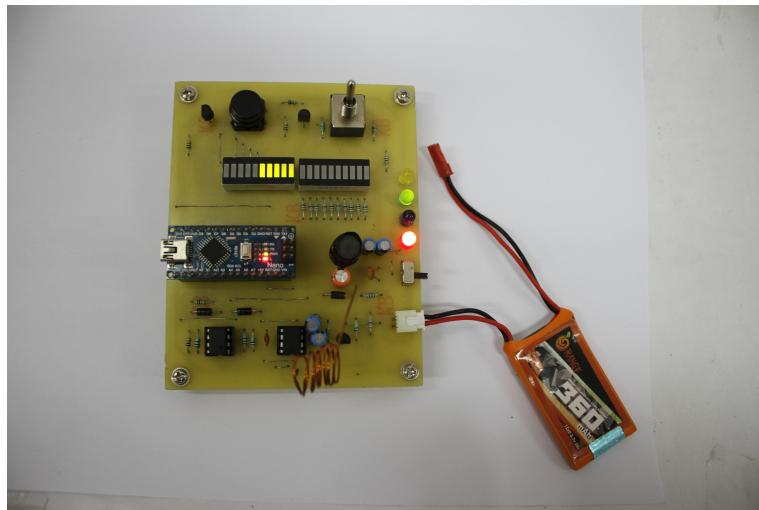


Figure 9: Electroscope with a positive charge in LOW gain Mode

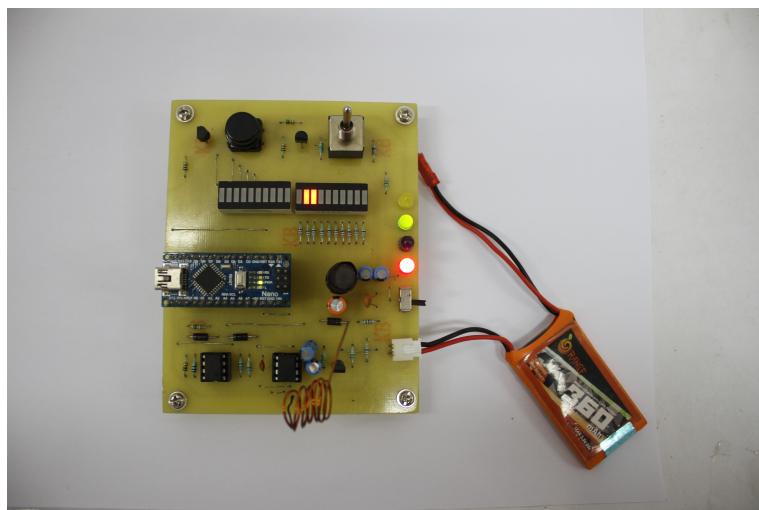


Figure 10: Electroscope with a negative charge in LOW gain Mode

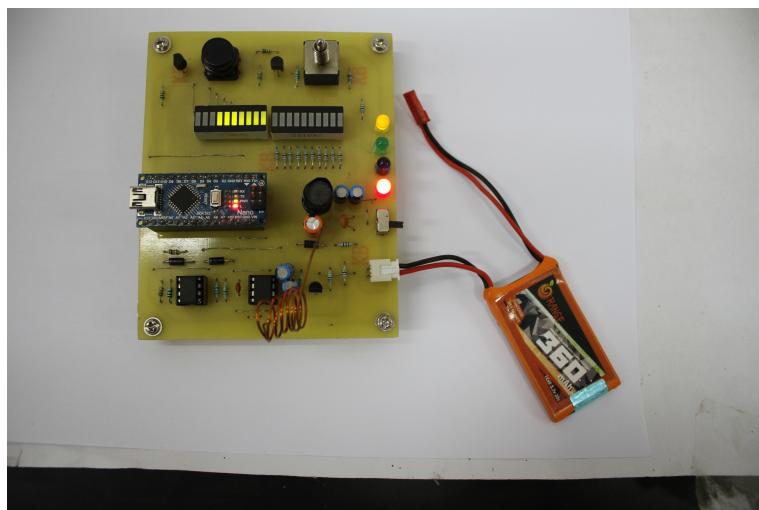


Figure 11: Electroscope with a positive charge in HIGH gain Mode

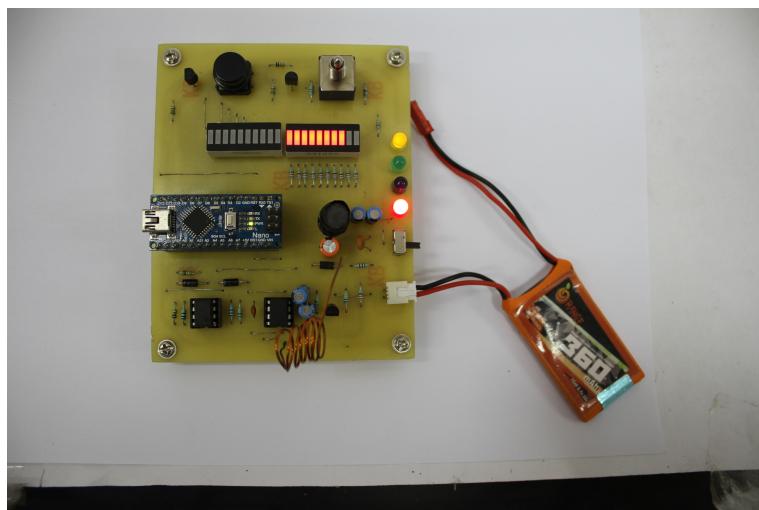


Figure 12: Electroscope with a negative charge in HIGH gain Mode

8. Bibliography

- Datasheet of TLC 272 BC
https://www.ti.com/lit/ds/symlink/tlc272.pdf?ts=1690783846438&ref_url=https%253A%252F%252Fwww.google.com%252F
- Datasheet of BL8530
<https://www.sunrom.com/download/456.pdf>
- Datasheet of TJ7660
<http://www.htckorea.co.kr/Datasheet/Converter-Controller/TJ7660.pdf>
- Charge sniffer for electrostatics demonstrations
https://www.researchgate.net/publication/253780812_Charge_sniffer_for_electrostatics_demonstrations
- Arduino NANO
<https://docs.arduino.cc/hardware/nano>
- An Electronic Electroscope
<https://iopscience.iop.org/article/10.1088/0031-9120/49/1/18/meta>